

Team #: \_\_\_\_\_  
 Absent: \_\_\_\_\_

Name: \_\_\_\_\_

1. Sum the following binary (base 2) numbers

$$\begin{array}{r} 10011_2 \\ +10110_2 \\ \hline \end{array}$$

$$\begin{array}{r} 101101_2 \\ +110111_2 \\ \hline \end{array}$$


2. Complete the Full-Adder truth table for the sum ( $s_i$ ) and carry-out ( $c_{i+1}$ ) functions.

$x_i$	$y_i$	carry-in $c_i$	sum $s_i$	carry-out $c_{i+1}$
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

3. Use k-maps to minimize the sum ( $s_i$ ) and carry-out ( $c_{i+1}$ ) functions of the Full-Adder:

4. For the one-bit Full-Adder, how many gate delays are needed before the carry-out ( $c_{i+1}$ ) wire is correct?

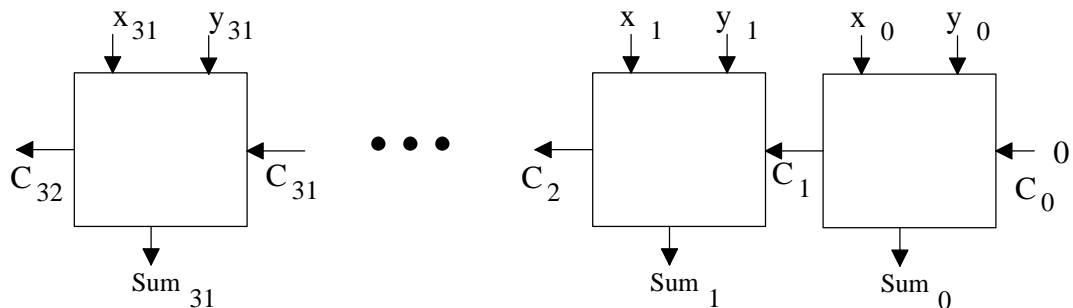5. A 32-bit, ripple-adder is made up of a collection of single-bit Full-Adders connected together as shown below:




How many gate delays are needed before  $c_{32}$  is correct?

Team #: \_\_\_\_\_  
 Absent: \_\_\_\_\_

Name: \_\_\_\_\_

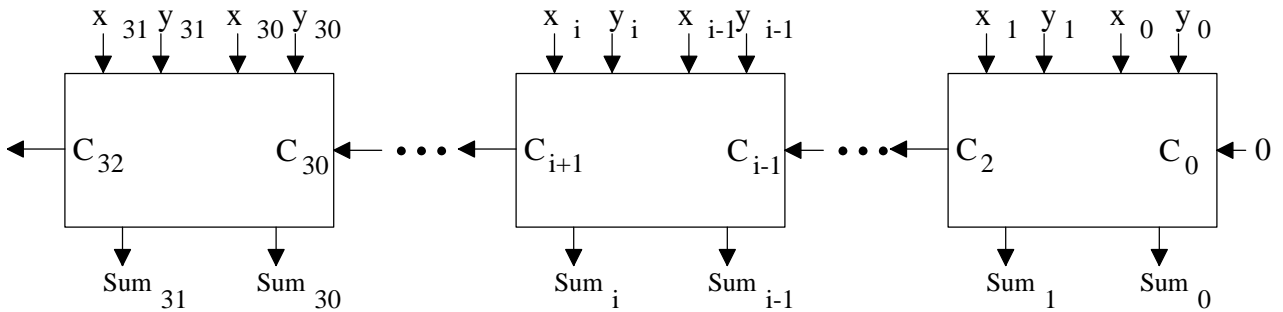6. To speed up the calculation of the carry-out ( $C_{i+1}$ ) signals, consider constructing a 32-bit adder using two-bit adders as shown in:



If  $c_{i+1}$  is calculated directly from the inputs as  $c_{i+1} = x_i y_i + x_i x_{i-1} y_{i-1} + x_i x_{i-1} c_{i-1} + x_i y_{i-1} c_{i-1} + y_i x_{i-1} y_{i-1} + y_i x_{i-1} c_{i-1} + y_i y_{i-1} c_{i-1}$ , then how many gate delays would be needed to calculate the  $c_{i+1}$  signal in a two-bit adder?

7. What would be the total number of gate delays in a 32-bit adder before the  $c_{32}$  signal is generated correctly if **two-bit adders** were used?

8. What would be the total number of gate delays in a 32-bit adder before the  $c_{32}$  signal is generated correctly if **three-bit adders** were used (10 three-bit adders and a 2-bit adder)?

9. What would be the total number of gate delays in a 32-bit adder before the  $c_{32}$  signal is generated correctly if **four-bit adders** were used?